

GATE-2023 (EE)


Q 29

MANOJ KUMAR (EE23BTECH11211)

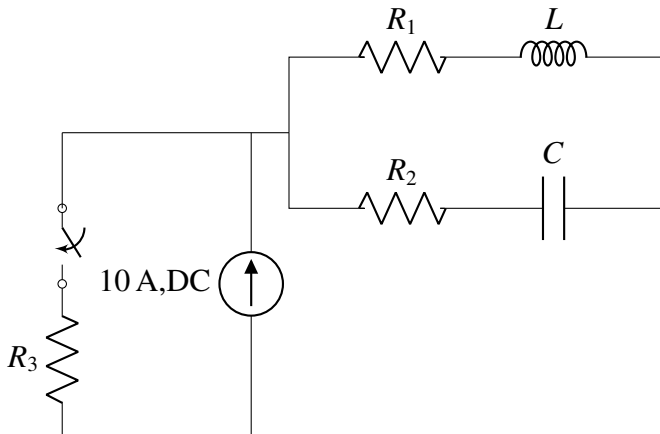Q29: The value of parameters of the circuit shown in the figure are

$$R_1 = 2\Omega, R_2 = 2\Omega, R_3 = 3\Omega, L = 10mH, C = 100\mu F$$

For time $t < 0$, the circuit is at steady state with the switch 'K' in closed condition. If the switch is opened at $t = 0$, the value of the voltage across the inductor (V_L) at $t = 0^+$ in Volts is _____ (Round off to 1 decimal place).




Solution:

Symbol	Value	Description
L	$10mH$	Inductance
C	$100\mu F$	Capacitance
R_1	2Ω	Resistance
R_2	2Ω	Resistance
R_3	3Ω	Resistance
V_L	??	Voltage across the inductor
V_C	??	Voltage across the capacitor
I_0	$10A$	DC current source
I_L	??	Current in inductor

TABLE 1: Input Parameter

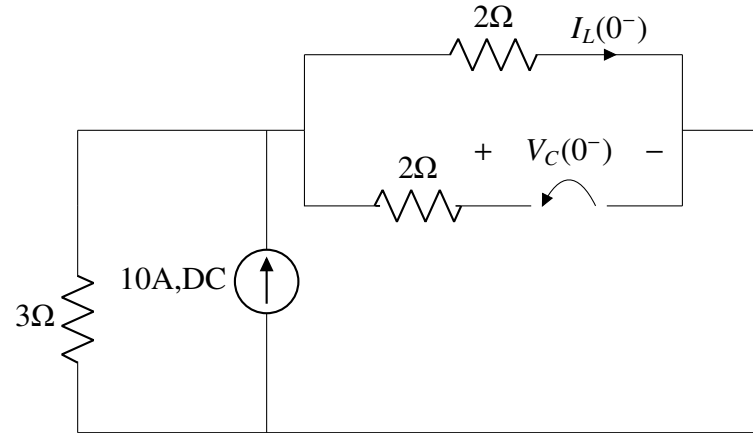At $t=0^-$, inductor behaves as wire and capacitor as open switch,




after current distribution

$$I_L(0^-) = 10A \left(\frac{3}{3+2} \right) = 6A \quad (1)$$

$$V_C(0^-) = 6 \times 2 = 12V \quad (2)$$

For $t > 0$, the switch is opened.

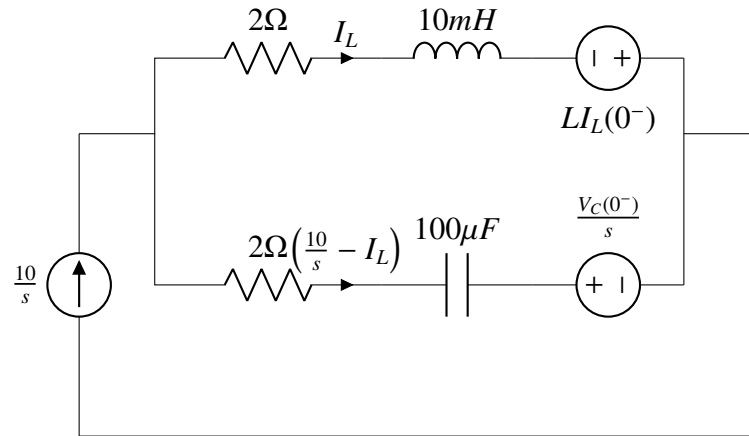

Using KVL,

$$2I_L + LsI_L - LI_L(0^-) - \frac{V_C(0^-)}{s} - \frac{1}{Cs} \left(\frac{10}{s} - I_L \right) - 2 \left(\frac{10}{s} - I_L \right) = 0 \quad (3)$$

From (1), (2), (3)

$$I_L = \frac{6s^2 + 3200s + 10^7}{s(s^2 + 400s + 10^6)} \quad (4)$$

$$V_L(s) = I_L(sL) \quad (5)$$

Using (4)

$$V_L(s) = \frac{0.06s^2 + 32s + 10^5}{(s^2 + 400s + 10^6)} \quad (6)$$

Some Result:

$$\frac{1}{s^2 + 400s + 10^6} \xleftrightarrow{\mathcal{L}} \left(e^{-200t} \right) \frac{\sin(400 \sqrt{6}t)}{400 \sqrt{6}} \quad (7)$$

$$\frac{s}{s^2 + 400s + 10^6} \xleftrightarrow{\mathcal{L}} \left(e^{-200t} \right) \frac{(2 \sqrt{6} \cos(400 \sqrt{6}t) - \sin(400 \sqrt{6}t))}{2 \sqrt{6}} \quad (8)$$

$$\frac{s^2}{s^2 + 400s + 10^6} \xleftrightarrow{\mathcal{L}} \left(-e^{-200t} \right) \frac{(2300 \sin(400 \sqrt{6}t) + 400 \sqrt{6} \cos(400 \sqrt{6}t))}{\sqrt{6}} \quad (9)$$

Inverse Laplace transform of (6) Using (7),(8),
(9)

$$V_L(t) = e^{-200t} \left(-0.06 \left(\frac{(2300 \sin(400 \sqrt{6}t) + 400 \sqrt{6} \cos(400 \sqrt{6}t))}{\sqrt{6}} \right) + 32 \left(\frac{(2 \sqrt{6} \cos(400 \sqrt{6}t) - \sin(400 \sqrt{6}t))}{2 \sqrt{6}} \right) \right) \\ + e^{-200t} \left(10^5 \frac{\sin(400 \sqrt{6}t)}{400 \sqrt{6}} \right) \quad (10)$$

at $t=0^+$

$$V_L(0^+) = -24 + 32 = 8V \quad (11)$$

Hence at $t=0^+$ voltage across inductor is 8V